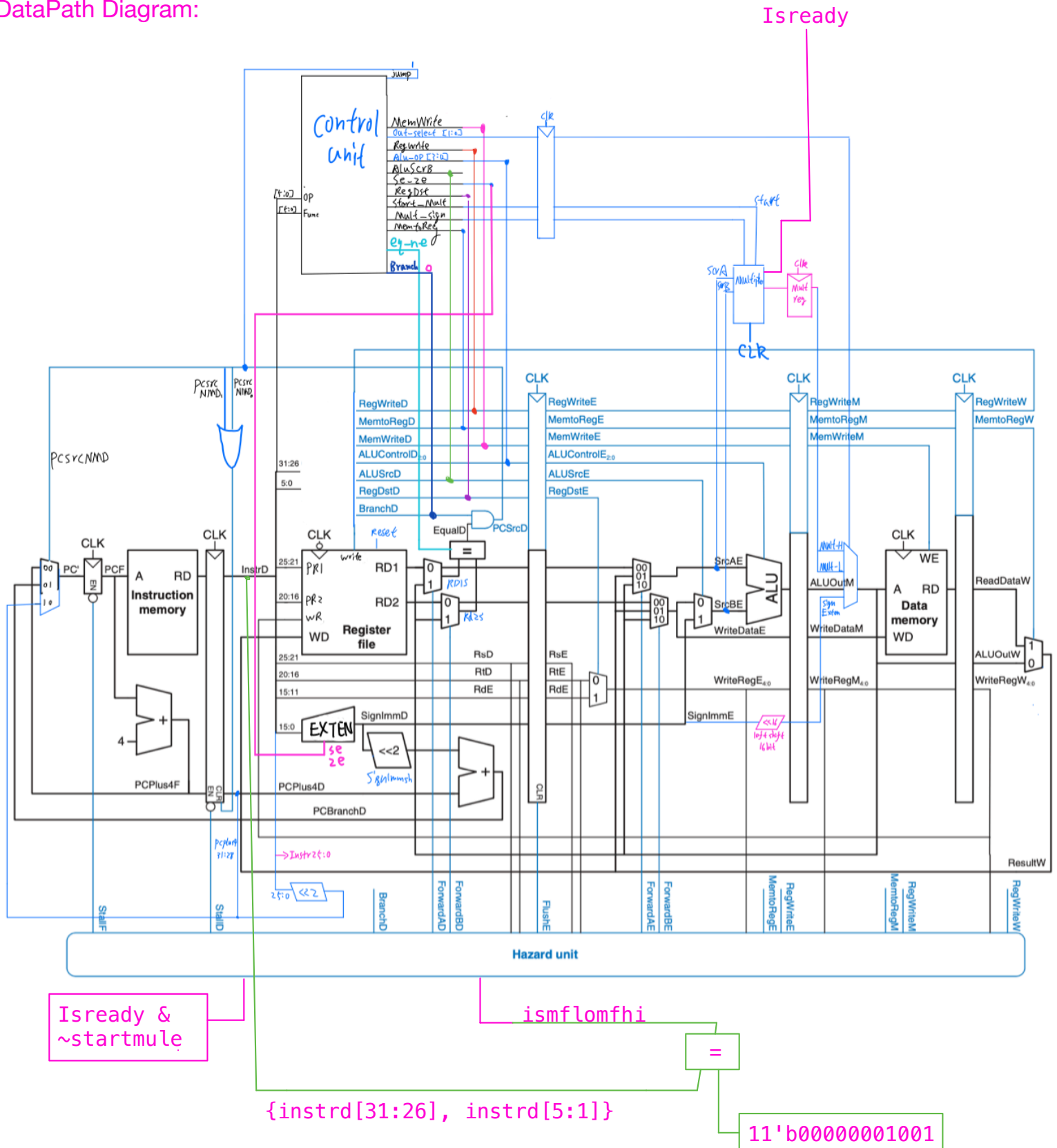



## DataPath Diagram:



The diagram above is the data path of our 5-stage pipeline mips processor.

memfile.dat is for question 1  
instrfile.dat is for question 2  
Ruozhifile.dat is for extra credit question  
multiple.dat is for multiplier  
Hazardfile.dat is for hazard unit


## ALU Module:

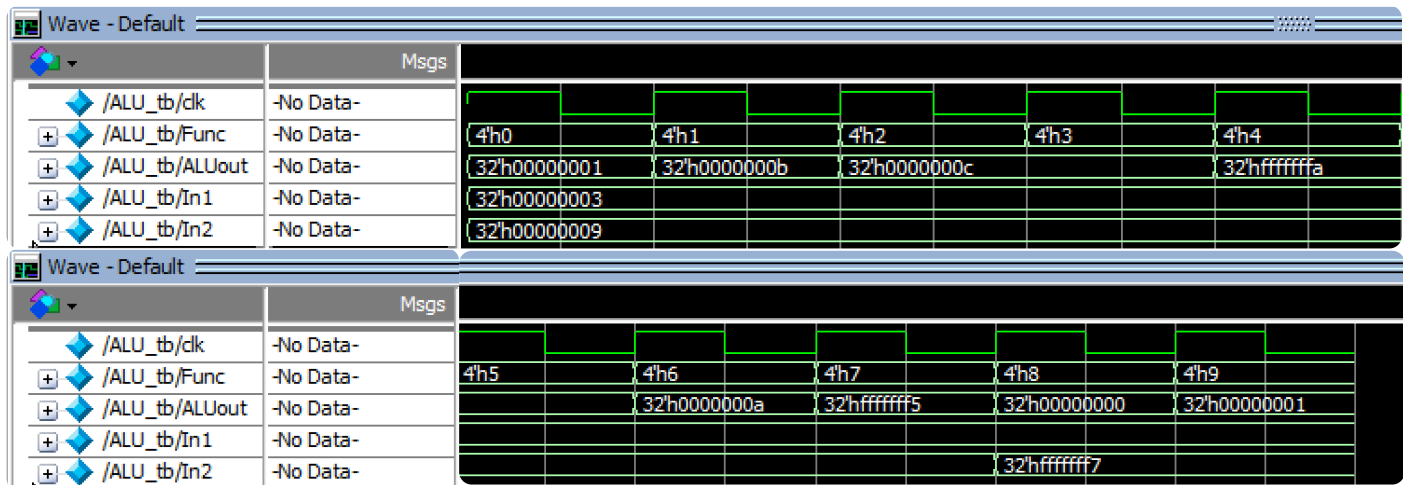


	A	B	C	D	E	F
1	operation	Func (binary)	Input1	input2	ALUout	cycle
2	and/andi	0000	0x3	0x9	0x1	1
3	or / ori	0001	0x3	0x9	0xb	2
4	add / addi	0010	0x3	0x9	0xc	3
5	addu / addiu	0011	0x3	0x9	0xc	4
6	sub	0100	0x3	0x9	0xfffffffffa	5
7	subu	0101	0x3	0x9	0xfffffffffa	6
8	Xor / Xori	0110	0x3	0x9	0xa	7
9	Xnor / Xnori	0111	0x3	0x9	0xfffffffff5	8
10	SLT / SLTi	1000	0x3	-0x9	0x0	9
11	SLTU / SLTiU	1001	0x3	0xfffffffff7	0x1	10

So based on our implementation of the func code, we can see that depending on the different Func Code we input with, we will see the ALU module is working perfectly with each function. For example, add operation  $3+9 = 12 = 0xc$ , and SLT 3 and 9,  $3 < 9$  and the result is 0. And if we use SLTU the result will be 1.

## Controller:

 


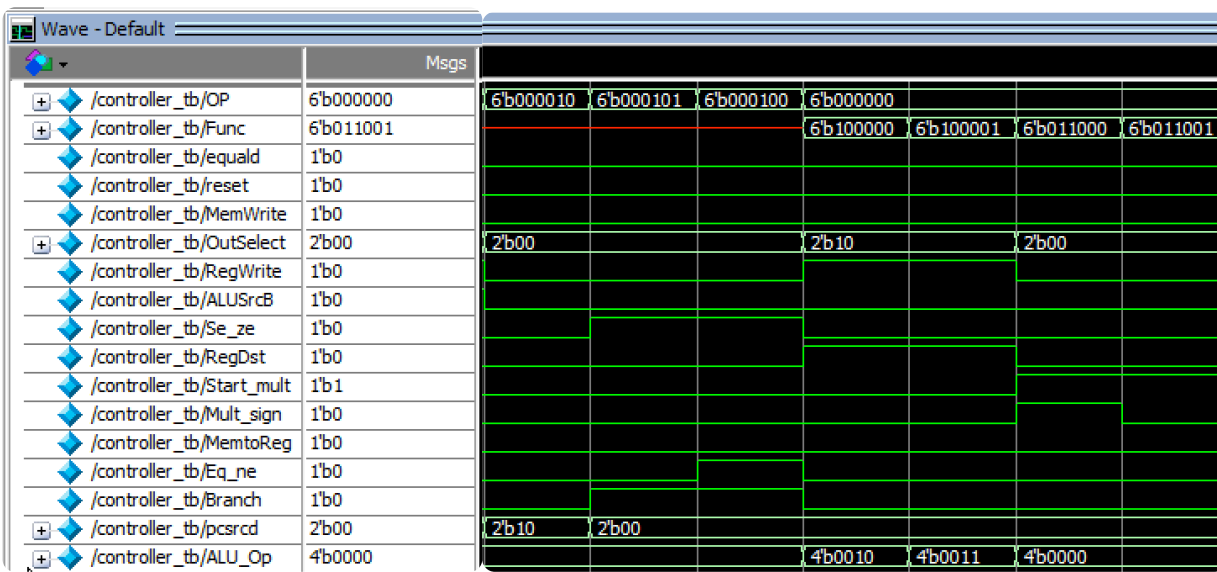

	A	B	C	D	E	F	G	H	I	J	K	L	M	N
	Command	memwrite	out_sel[1:0]	RegWrite	aluSrcB	se_ze	RegDst[1:0]	start_mult	mult_sign	memtoReg	eq_ne	branch	pcsrcD	alu_op[3:0]
1	addi	0	10	1	1	1	10	0	0	0	x	x	00	0010
2	addi	0	10	1	1	1	10	0	0	0	x	x	00	0011
3	andi	0	10	1	1	0	10	0	0	0	x	x	00	0000
4	ori	0	10	1	1	0	10	0	0	0	x	x	00	0001
5	xori	0	10	1	1	0	10	0	0	0	x	x	00	0110
6	slti	0	10	1	1	1	10	0	0	0	x	x	00	1000
7	sltiu	0	10	1	1	1	10	0	0	0	x	x	00	1001
8	lw	0	10	1	1	1	10	0	0	1	x	x	00	0010
9	sw	1	10	0	1	1	x	0	0	x	x	x	00	0010
10	lui	0	11	1	1	0	10	0	0	0	x	x	00	x
11	j	0	x	0	x	x	x	0	0	x	x	x	10	x
12	bne	0	x	0	x	1	x	0	0	x	0	1	01	x
13	beq	0	x	0	x	1	x	0	0	x	1	1	01	x
14														
15														
16														
17	add	0	10	1	0	x	11	0	0	0	x	x	00	0010
18	addu	0	10	1	0	x	11	0	0	0	x	x	00	0011
19	sub	0	10	1	0	x	11	0	0	0	x	x	00	0100
20	subu	0	10	1	0	x	11	0	0	0	x	x	00	0101
21	and	0	10	1	0	x	11	0	0	0	x	x	00	0000
22	or	0	10	1	0	x	11	0	0	0	x	x	00	0001
23	xor	0	10	1	0	x	11	0	0	0	x	x	00	0110
24	xnor	0	10	1	0	x	11	0	0	0	x	x	00	0111
25	slt	0	10	1	0	x	11	0	0	0	x	x	00	1000
26	sltu	0	10	1	0	x	11	0	0	0	x	x	00	1001
27	mult	0	xx	0	0	x	xx	1	0	0	x	x	00	x
28	multu	0	xx	0	0	x	xx	1	1	0	x	x	00	x
29	mfhi	0	00	1	x	x		11	0 0	0	x	x	00	xxxx
30	mflo	0	01	1	x	x		11	0 0	0	x	x	00	xxxx


As the waveform shown above, it is a decoder that decode the instruction code and operation code to each port, and corresponding to our decoding table, the values are correct.

## Data\_Memory Module

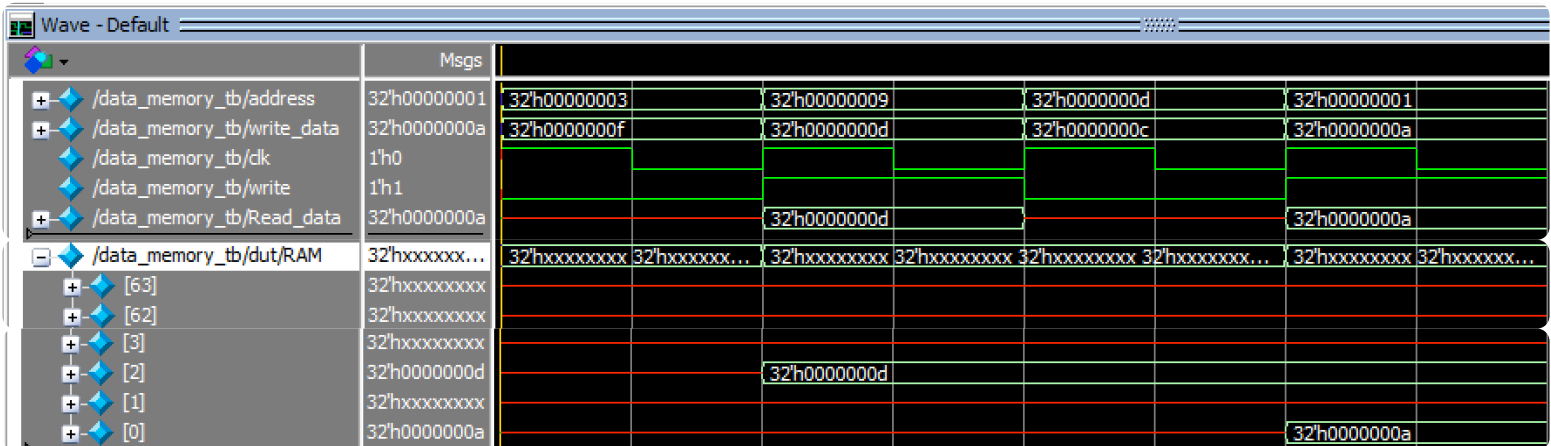


Data memory is used for LW and SW operation, which will write or load data into the address we specified and the 'write' signal should be enabled in order to write in data. So we can see in the wave form, whenever the 'write' signal is enabled, the data will be stored in data memory. For the address, we ignore the last two bit of the address we give. For example, above we assign the address as 32'b 1001, so the address corresponding in RAM is 32'b 10 witch is address 2.

### Instruction memory module:

 


For the instruction memory module, we read these three instruction,  
 addi t2 zero 26;  
 addi t3 zero -20;  
 addi, \$t0, \$0, 28;  
 and the corresponding hex code are:  
 200a001a  
 200bfffec  
 2008001c  
 so we can see the read\_data was matched our instruction correctly. So the module works perfectly.


### Reg file module:

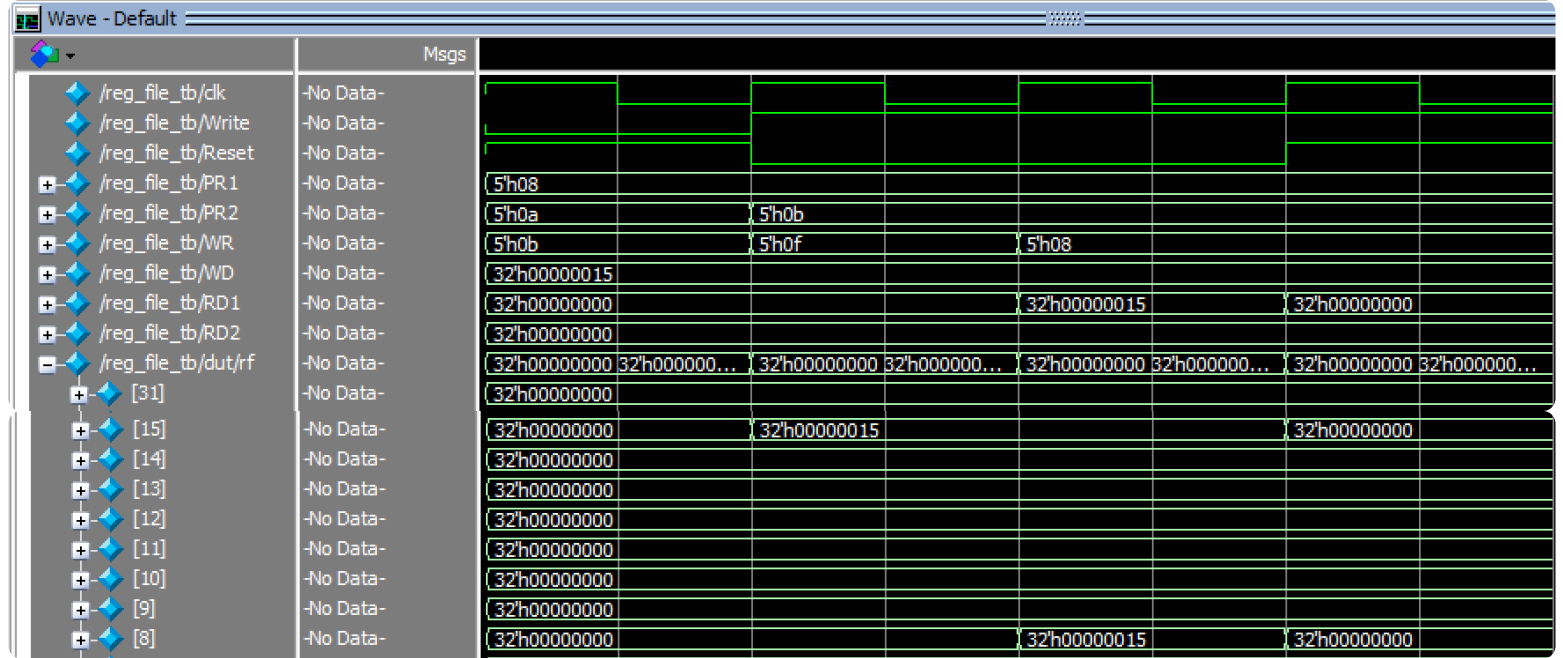

For the reg\_file module, we can see there first set the Writdata (WD) to 0x15, and only if the Wirte signal is enabled we can store the data into the register file (rf) in the address we specified as 0xb which is 15 in the rf. Same for the later operations. So our Reg-File register also works correctly.





### Multiplier Module:

 

 

For the multiplier module, from the wave form, we can see that our multiplier was finish with the calculation when the laji\_counter become to 0, and therefore our multiplier is using 32 cycles to calculate out the result. Also in order to do the 'mult' 'mflw' and 'mfhi' command sequently, we assigned a 'isready' signal to hazard unit for stalling.

    Following are more operations we test and the result are correctly. ( numbers shows in decimal )



Hazard unit module:


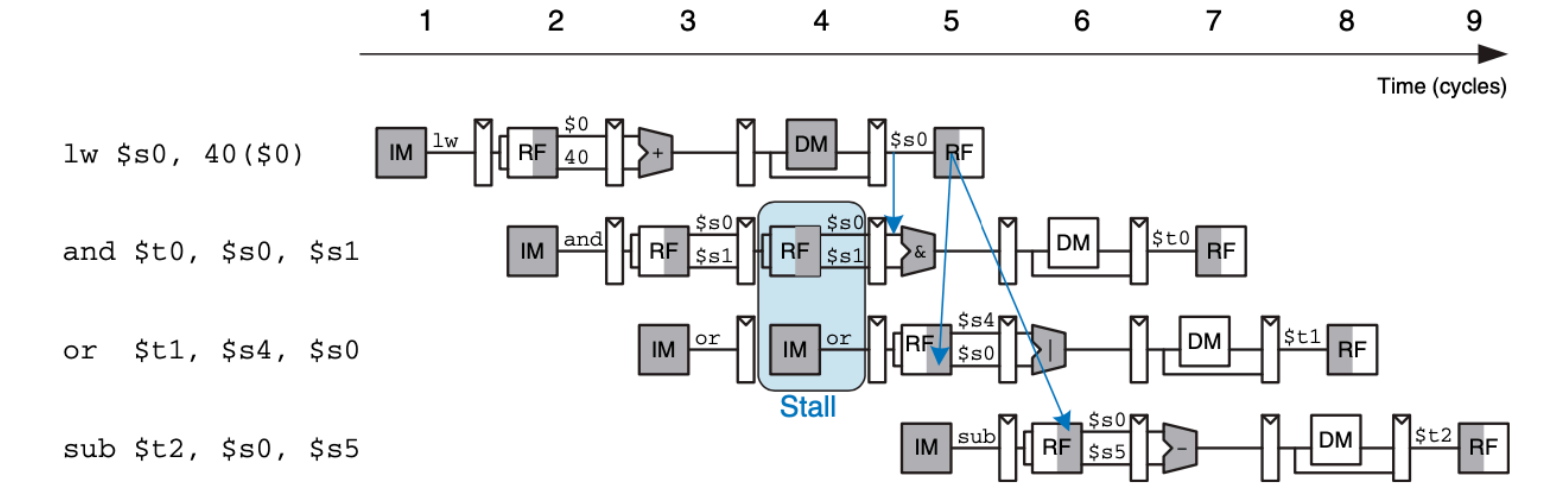


Figure 7.52 Abstract pipeline diagram illustrating stall to solve hazards

 

We test our hazard module by doing the above command, and we can see the stallF and stallD happened when we want to use the result from LW instruction right after LW instruction. ( the hazardfile.dat in our files is the program we used here).


And the forward happened in the write stage, and forward the data directly to the decode stage. We can see in 50ns the forward AD was enabled, because in here we can see in the graph above it forward the data to the or and sub instruction.






## Final Test: (for question 1)

#	Assembly	Description	Address	Machine	
main:	addi \$2, \$0, 5	# initialize \$2 = 5	0	20020005	20020005
	addi \$3, \$0, 12	# initialize \$3 = 12	4	2003000c	2003000c
	addi \$7, \$3, -9	# initialize \$7 = 3	8	2067fff7	2067fff7
	or \$4, \$7, \$2	# \$4 = (3 OR 5) = 7	c	00e22025	00e22025
	and \$5, \$3, \$4	# \$5 = (12 AND 7) = 4	10	00642824	00642824
	add \$5, \$5, \$4	# \$5 = 4 + 7 = 11	14	00a42820	00a42820
	beq \$5, \$7, end	# shouldn't be taken	18	10a7000a	10a7000a
	slt \$4, \$3, \$4	# \$4 = 12 < 7 = 0	1c	0064202a	0064202a
	beq \$4, \$0, around	# should be taken	20	10800001	10800001
	addi \$5, \$0, 0	# shouldn't happen	24	20050000	20050000
around:	slt \$4, \$7, \$2	# \$4 = 3 < 5 = 1	28	00e2202a	00e2202a
	add \$7, \$4, \$5	# \$7 = 1 + 11 = 12	2c	00853820	00853820
	sub \$7, \$7, \$2	# \$7 = 12 - 5 = 7	30	00e23822	00e23822
	sw \$7, 68(\$3)	# [80] = 7	34	ac670044	ac670044
	lw \$2, 80(\$0)	# \$2 = [80] = 7	38	8c020050	8c020050
	j end	# should be taken	3c	08000011	08000011
	addi \$2, \$0, 1	# shouldn't happen	40	20020001	20020001
end:	sw \$2, 84(\$0)	# write mem[84] = 7	44	ac020054	ac020054
	MULT \$v0 \$a3			00470018	
	MFLO \$s1			00008812	
	MFHI \$s0			00008010	
	LUI \$s2 0x0029			3C120029	

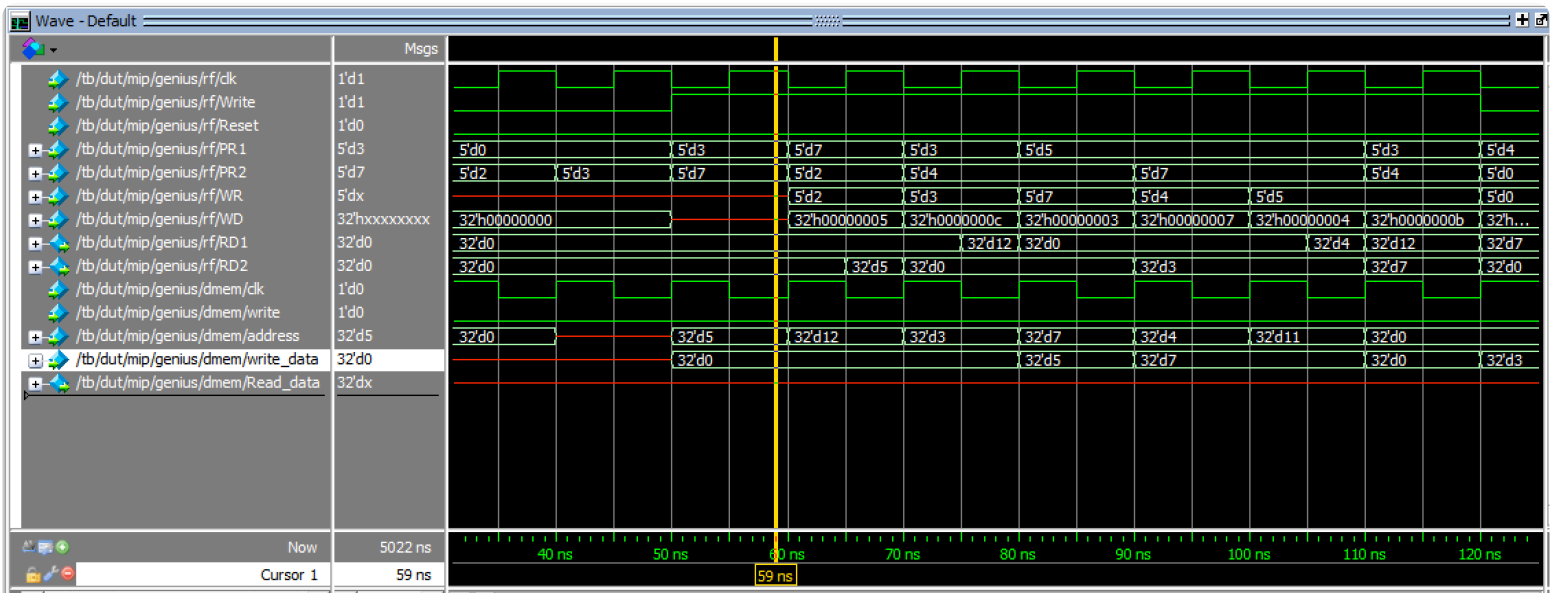
Above is our final test program and the wave form is shown in below:



   

 Here is a 31 cycles stall for the multi instruction





For question 2:

```
addi, $t0, $0, 28;      2008001c
addi, $t1, $0, -240;    2009FF10
mult, $t0, $t1;         01090018
mflo $t3;              00005812
add $t5,$t3,$0;        01606820
```

```
addi $t0, $0, 110;      2008006E
addi $t1, $0, 91;       2009005B
mult $t0, $t1;          01090018
mflo $t3;              00005812
add $t5,$t5,$t3;       01AB6820
```




```
addi $t0, $0, -67;      2008FFD7
addi $t1, $0, 88;       2009FF9B
mult $t0, $t1;          01090018
mflo $t3;              00005812
add $t5,$t5,$t3;       01AB6820
```

```
addi $t0, $0, -41;      20080017
addi $t1, $0, -101;     20090096
mult $t0, $t1;          01090018
mflo $t3;              00005812
add $t5,$t5,$t3;       01AB6820
```

```
addi $t0, $0, 23;       2008FFBD
addi $t1, $0, 150;      20090058
mult $t0, $t1;          01090018
mflo $t3;              00005812
add $t5,$t5,$t3;       01AB6820
```

this is the code we run for the dot product.

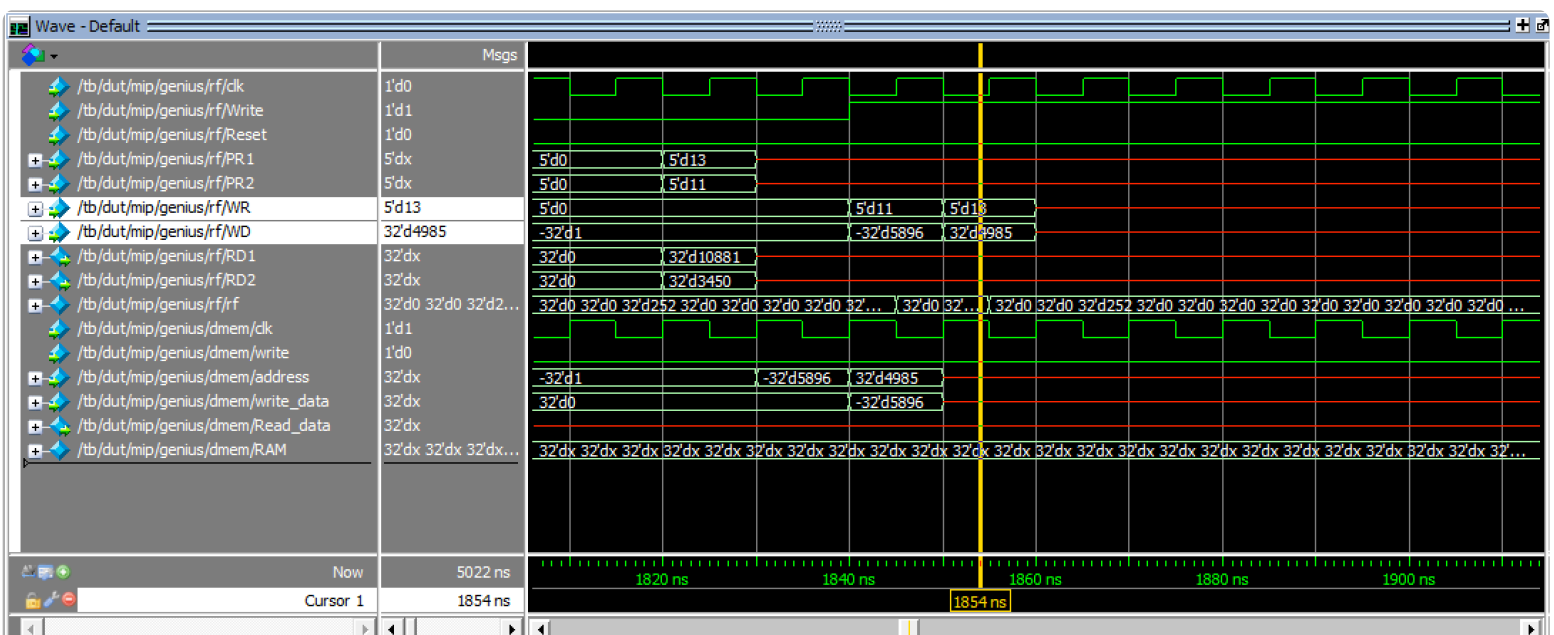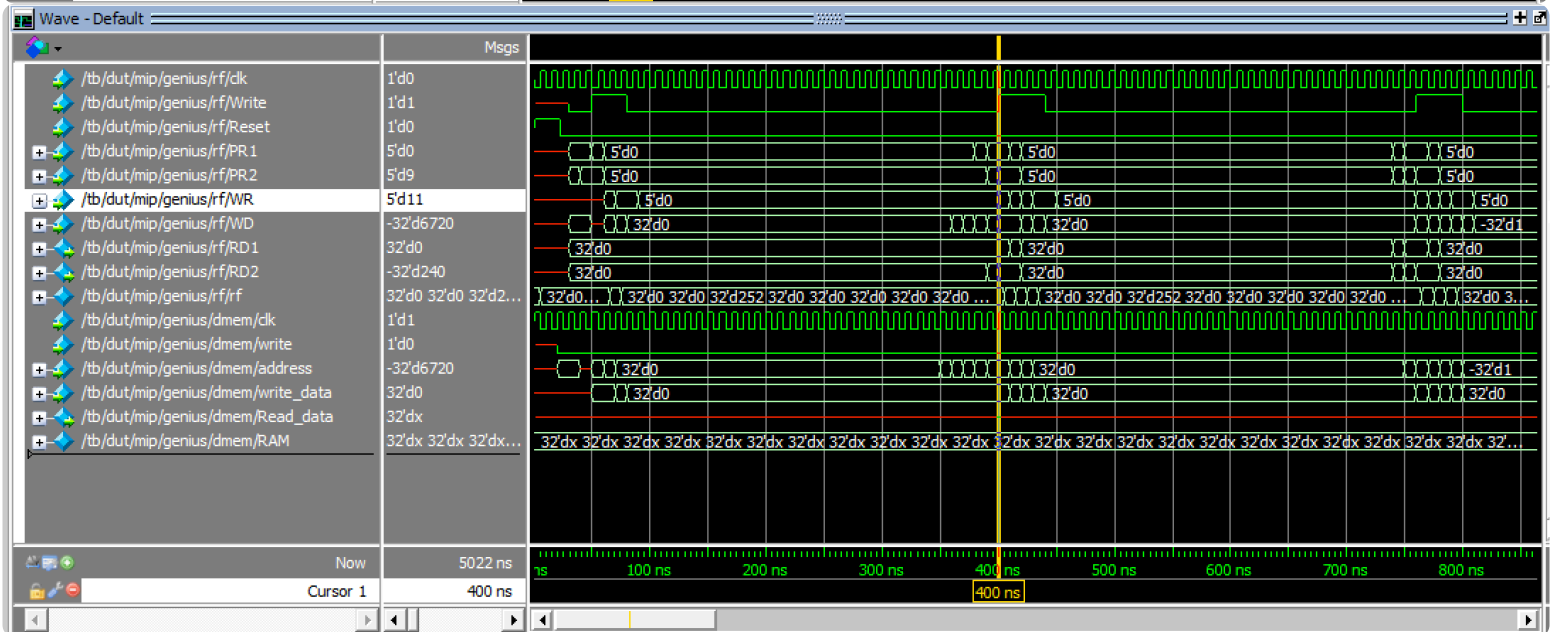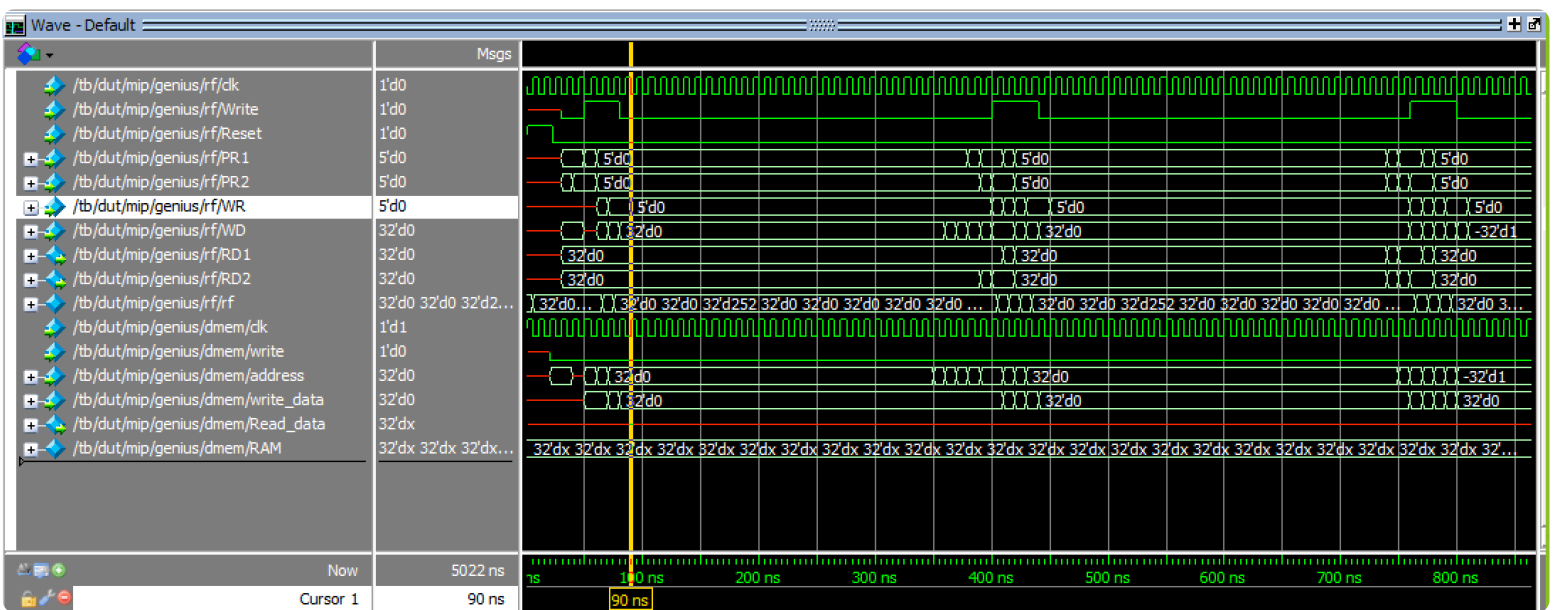For our program, it take 184 cycles to calculate out the result.



From these two figures we can find the our processor will stall 31 cycles for each multiplication.

And we got the result as 4985 witch is a correct answer.

## Extra Credit:

For the extra credit, we implement the instruction in the following way

main:

```
ori $t0, $zero, 3;
sw $t0, 0($zero);
ori $t0, $zero, 84;
sw $t0, 4($zero);
ori $t0, $zero, 93;
sw $t0, 8($zero);
ori $t0, $zero, 67;
sw $t0, 12($zero);
ori $t0, $zero, 75;
sw $t0, 16($zero);
ori $t0, $zero, 74;
sw $t0, 20($zero);
ori $t0, $zero, 39;
sw $t0, 24($zero);
ori $t0, $zero, 65;
sw $t0, 28($zero);
ori $t0, $zero, 17;
sw $t0, 32($zero);
ori $t0, $zero, 70;
sw $t0, 36($zero);
ori $t0, $zero, 3;
sw $t0, 40($zero);
```

```
ori $t0, $zero, 27;
sw $t0, 44($zero);
ori $t0, $zero, 4;
sw $t0, 48($zero);
ori $t0, $zero, 9;
sw $t0, 52($zero);
ori $t0, $zero, 82;
sw $t0, 56($zero);
ori $t0, $zero, 69;
sw $t0, 60($zero);
ori $t0, $zero, 31;
sw $t0, 64($zero);
ori $t0, $zero, 95;
sw $t0, 68($zero);
ori $t0, $zero, 3;
sw $t0, 72($zero);
ori $t0, $zero, 43;
sw $t0, 76($zero);
ori $t0, $zero, 38;
sw $t0, 80($zero);
ori $t0, $zero, 76;
sw $t0, 84($zero);
```

These are store the array in the memory  
x = [3, 84, 93, 67, 75, 74, 39, 65, 17, 70, 3];  
y = [27, 4, 9, 82, 69, 31, 95, 3, 43, 38, 76];  
x is stored in memory address 0 to 40;  
y is stored in memory address 44 to 84;


// our program start here

```
ori $t0, $zero, 0;
ori $t1, $zero, 40;
ori $t2, $zero, 44;
```


laji:

```
lw $t3, 0($t0);
lw $t4, 0($t2);
add $t5, $zero, $t3;
add $t5, $t5, $t3;
add $t5, $t5, $t3;
add $t5, $t5, $t3;
add $t5, $t5, $t3;
add $t5, $t5, $t4;
sw $t5, 4($t2);
addi $t0, $t0, 4;
addi $t2, $t2, 4;
bne $t0, $t1, laji
```

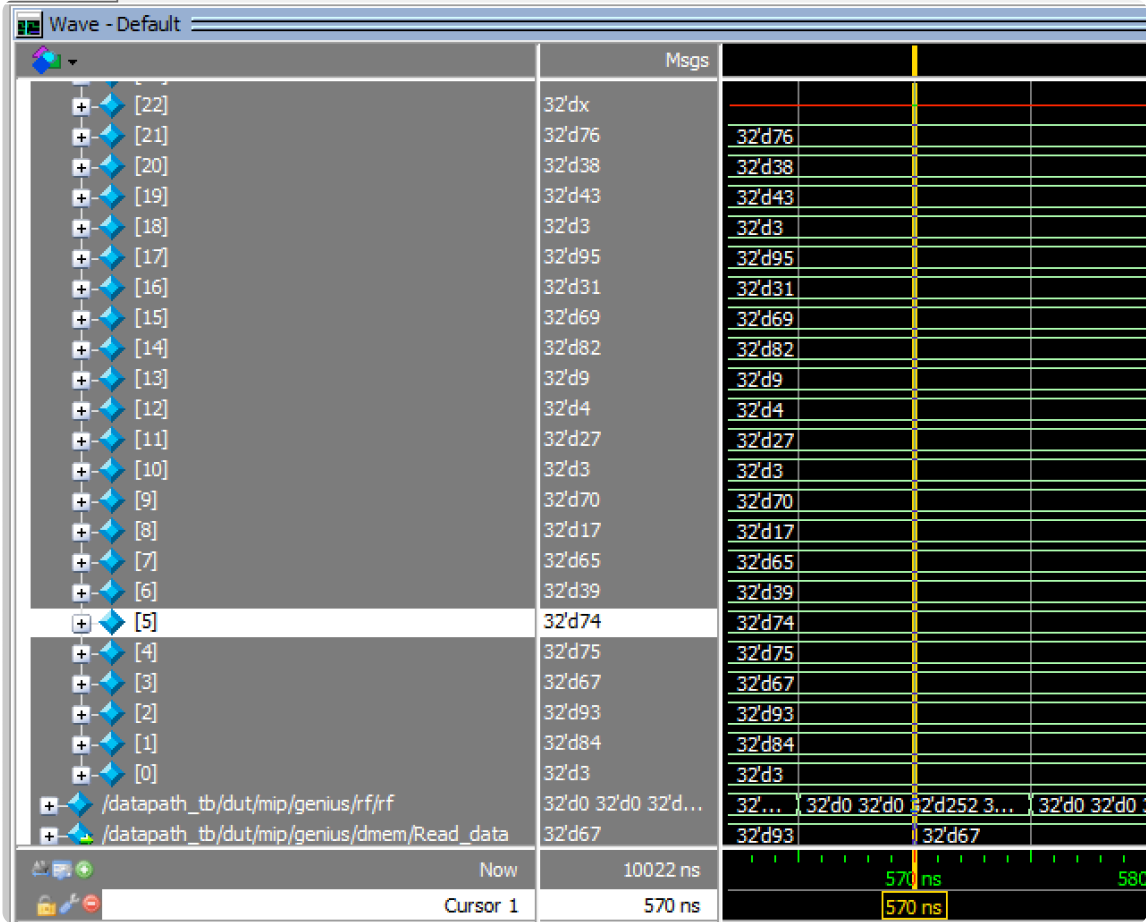Before: two arrays are stored in the memory showing in below



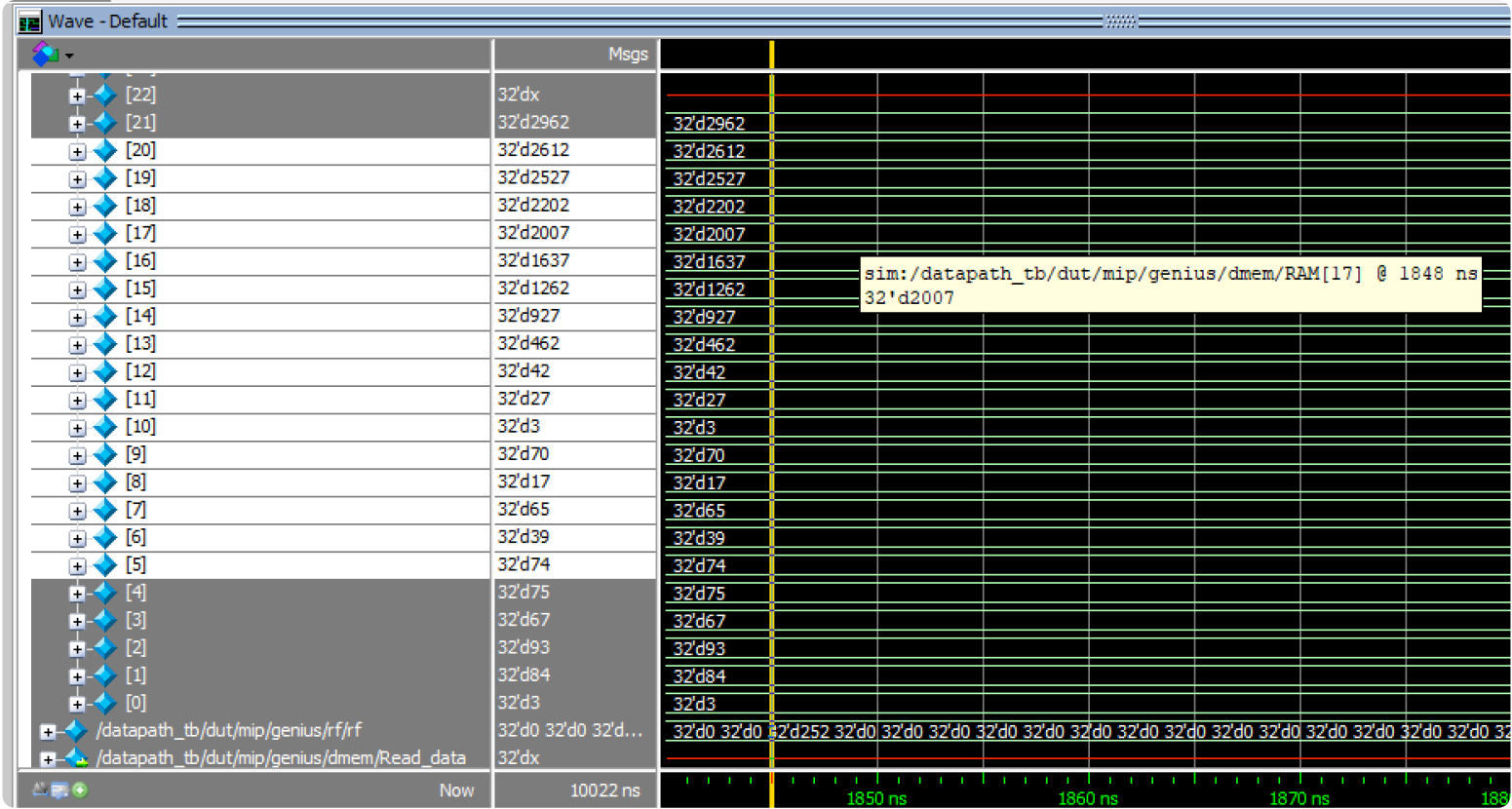After: the array of value was changed: y is [27, 42, 462, 927, 1262, 1637,2007,2527, 2612, 2962]



Then we verified it with writing a python program and check the result

```
1 x = [3, 84, 93, 67, 75, 74, 39, 65, 17, 70, 3];
2 y = [27, 4, 9, 82, 69, 31, 95, 3, 43, 38, 76];
3
4 for i in range (0,10):
5     y[i+1] = 5*x[i]+y[i]
6
7
8
9 for j in range (0,11):
10    print(y[j])
```

The output is shown in below which is exactly match our output:

```
27
42
462
927
1262
1637
2007
2202
2527
2612
2962
```

## Code:

### ALU.v:

```
module ALU (input [31:0] In1, In2, input [3:0] Func,
            output reg [31:0] ALUout);
    //wire [31:0] BB;
    wire [31:0] S;
    wire [31:0] Sub;
    wire y2;
    wire y;
    wire cout;
    wire [31:0] US;

    //assign BB = (Func[3]) ? ~In2 : In2;
    assign {cout, S} = In1 + In2; //was bb signed
    assign {cout, Sub} = In1 + ~In2 + 1;
    assign y = (In1[31:31] > In2[31:31]) || ((In1[31:31] == 0 && In2[31:31] == 0 && In1[30:0] < In2[30:0]) || ((In1[31:31] == 1 && In2[31:31] == 1 && In1[30:0] > In2[30:0])) ? 32'b1:32'b0;
    assign y2 = (In1 < In2) ? 32'b1 : 32'b0;
    always @ * begin
        case (Func[3:0])
            4'b0000 : ALUout <= In1 & In2; //and / andi
            4'b0001 : ALUout <= In1 | In2; //or and ori
            4'b0010 : ALUout <= S; //add and addi
            4'b0011 : ALUout <= Sub;
            4'b0100 : ALUout <= Sub; // sub
            4'b0101 : ALUout <= Sub; // subu
            4'b0110 : ALUout <= In1 ^ In2; // Xor ,Xori
            4'b0111 : ALUout <= In1 ^~ In2; // Xnor ,Xnori
            4'b1000 : ALUout <= y; //SLT, SLTi
            4'b1001 : ALUout <= y2; //SLTU, SLTiU
        endcase
    end
```

```
end
endmodule
```

## ALU\_tb.v:

```
module ALU_tb();
    reg clk;
    reg [3:0] Func;
    wire [31:0] ALUout;
    reg [31:0] In1, In2;
    ALU dut(In1, In2, Func, ALUout);
    always begin
        clk <= 1;#5;clk<=0;#5;
    end
    initial begin
        In1 <= 32'b0011;
        In2 <= 32'b1001;
        Func <= 4'b0000;
        #10
        Func <= 4'b0001;
        #10
        Func <= 4'b0010;
        #10
        Func <= 4'b0011;
        #10
        Func <= 4'b0100;
        #10
        Func <= 4'b0101;
        #10
        Func <= 4'b0110;
        #10
        Func <= 4'b0111;
        #10
        In2 <= -32'b1001;
        Func <= 4'b1000;
        #10
        In2 <= -32'b1001;
        Func <= 4'b1001;
        #10

        $stop;
    end
end
endmodule
```

## Controller.v:

```
module Controller (input EqualD, input [5:0] OP,input [5:0] Func, /*input clk,*/ input reset, output MemWrite, /*output jump,*/
    output [1:0] OutSelect, output RegWrite, output ALUSrcB, output Se_ze, output RegDst,
    output Start_mult, output Mult_sign, output MemtoReg, output Eq_ne, output Branch, output [1:0] PCSrcD, output [3:0] ALU_Op);

    reg [16:0] controls;
    wire jump;

    assign {jump,MemWrite, OutSelect, RegWrite, ALUSrcB, Se_ze, RegDst,Start_mult, Mult_sign, MemtoReg, Eq_ne, Branch,
    ALU_Op} = controls;
    assign PCSrcD = {jump, (Branch&EqualD)};

    always @* begin
        if (reset) begin
            controls <= 17'b0;
        end else begin

            case(OP)
                6'b001000: controls <= 17'b001011100000000010; // addi
                6'b001001: controls <= 17'b001011100000000011; // addiu
                6'b001100: controls <= 17'b001011000000000000; // andi
```

```

6'b001101: controls <= 17'b00101100000000001; // ori
6'b001110: controls <= 17'b001011000000000110; // xori
6'b001010: controls <= 17'b001011100000001000; // slti
6'b001011: controls <= 17'b001011100000001001; // sltiu
6'b100011: controls <= 17'b001011100010000010; // lw
6'b101011: controls <= 17'b011001100000000010; // sw
6'b001111: controls <= 17'b001111000000000000; // lui
6'b000010: controls <= 17'b100000000000000000; // j
6'b000101: controls <= 17'b000000010000010000; // bne
6'b000100: controls <= 17'b000000010000110000; // beq
default:
    case(Func)
        6'b100000: controls <= 17'b001010010000000010; //add
        6'b100001: controls <= 17'b001010010000000011; //addu
        6'b100010: controls <= 17'b001010010000000100; //sub
        6'b100011: controls <= 17'b001010010000000101; //subu
        6'b100100: controls <= 17'b001010010000000000; //and
        6'b100101: controls <= 17'b001010010000000001; //or
        6'b100110: controls <= 17'b001010010000000110; //xor
        6'b101010: controls <= 17'b001010010000001000; //slt
        6'b101011: controls <= 17'b001010010000001001; //sltu
        6'b011000: controls <= 17'b000000000110000000; //mult
        6'b011001: controls <= 17'b000000000100000000; //multu
        6'b010000: controls <= 17'b000001001000000000; //mfhi
        6'b010010: controls <= 17'b000011001000000000; //mflo
        default: controls <= 17'b001010010000000111; //xnor
    endcase
endcase
end
endmodule

```

## controller\_tb.v:

```

module controller_tb();
    reg [5:0] OP;
    reg [5:0] Func;
    //reg clk;
    reg equald;
    reg reset;
    wire MemWrite;
    //wire jump;
    wire [1:0] OutSelect;
    wire RegWrite;
    wire ALUSrcB;
    wire Se_ze;
    wire RegDst;
    wire Start_mult;
    wire Mult_sign;
    wire MemtoReg;
    wire Eq_ne;
    wire Branch;
    wire [1:0] pcsrcd;
    wire [3:0] ALU_Op;

    Controller dut(equald,OP,Func,/*clk,*/reset,MemWrite,/*jump,*/
        OutSelect,RegWrite, ALUSrcB, Se_ze,RegDst,
        Start_mult,Mult_sign, MemtoReg, Eq_ne, Branch, pcsrcd,ALU_Op);
    /*always begin
        clk <= 1;#5;clk<=0;#5;
    end*/
    initial begin
        equald <=0;
        reset <= 0;
        OP <= 6'b001000; //addi
        #10;
    end
endmodule

```



```

OP <= 6'b001001; //andi
#10;
OP <= 6'b001100; // andi
#10;
OP <= 6'b001101; //ori
#10;
OP <= 6'b001110; //xori
#10;
OP <= 6'b001010; // slti
#10;
OP <= 6'b001011; // sltiu
#10;
OP <= 6'b100011; // lw
#10;
OP <= 6'b101011; //sw
#10;
OP <= 6'b001111; //lui
#10;
OP <= 6'b000010; //jump
#10;
OP <= 6'b000101; //bne
#10;
OP <= 6'b000100; //beq
#10;

//R type
OP <= 6'b0;
Func <= 6'b100000; //add
#10;
Func <= 6'b100001; //addu
#10;
Func <= 6'b011000; //mult
#10;
Func <= 6'b011001; //multu
#10;

```

```

$stop;

```

```

end
endmodule

```

## data\_memory.v:

```

module data_memory(input      clk, write,
input  [31:0] address, write_data,
output [31:0] Read_data);

```

```

// **PUT YOUR CODE HERE**
reg [31:0] RAM[63:0];

```

```

assign Read_data = RAM[address[31:2]]; //word aligned

```

```

always @(posedge clk) begin
    if (write) RAM[address[31:2]] <= write_data;
end
endmodule

```

```

// Instruction memory (already implemented)
module inst_memory(input  [31:0] address,
output [31:0] Read_data);

```

```

reg [31:0] RAM[63:0];

```

```

initial
begin
    $readmemh("memfile.dat",RAM); // initialize memory with test program. Change this with memfile2.dat for the modified code
end

```

```

    assign Read_data = RAM[address[31:2]]; // word aligned
endmodule

```

## Data\_memory\_tb.v:

```

module data_memory_tb();
    reg [31:0] address;
    reg [31:0] write_data;
    reg clk;
    reg write;
    wire [31:0] Read_data;
    data_memory dut(clk, write,address, write_data, Read_data);
    always begin
        clk <= 1;#5;clk<=0;#5;
    end
    initial begin
        write <= 0;
        address <= 32'b0011;
        write_data <= 32'b1111;
        #10
        write <= 1;
        address <= 32'b1001;
        write_data <= 32'b1101;
        #10
        write <=0;
        address <= 32'b1101;
        write_data <= 32'b1100;
        #10
        write <=1;
        address <= 32'b0001;
        write_data <= 32'b1010;
        #10
        $stop;
    end
endmodule

```

## inst\_memory\_tb.v:

```

module inst_memory_tb();
    reg [31:0] address;

    wire [31:0] Read_data;
    inst_memory dut(address, Read_data);

    initial begin
        #5;
        address <= 32'b0;
        #5;
        address <= 32'b100;
        #5;
        address <= 32'b1000;
        #5;

        $stop;
    end
endmodule

```

## GeneralMoudle.v:

```

//two input adder
module adder(input [31:0] a, b,
    output [31:0] y);
    assign y = a+b;
endmodule

```

```

// 64bit adder

```

```

module adder64(input [63:0] a,b,
               output [63:0] y);
    assign y = a+b;
endmodule

//shift module
module sl2(input [31:0] a,
           output [31:0] y);
    assign y = {a[29:0], 2'b00};
endmodule

module s25l2(input [25:0] a,
             output [27:0] y);
    assign y = {a[23:0], 2'b00};
endmodule

//shift 16bit
module sl16(input [31:0] a,
            output [31:0] y);
    assign y = {a[15:0],16'b0};// left shift 16
endmodule

module sl2jump(input [25:0] a,
               output [27:0] y);
    assign y = {a, 2'b00};
endmodule

//extention module can choose whether sign extend or zero extend
module extend(input [15:0] a,
              input se_ze,
              output [31:0] immext);
    assign immext = se_ze? {{16{a[15]}}, a}:{16'b0,a};
endmodule

//sign extention module
module signext(input [15:0] a,
               output [31:0] y);
    assign y = {{16{a[15]}}, a};
endmodule

//register
module flopr #(parameter WIDTH=8)
    (input clk, reset, enable,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk, posedge reset) begin
        if(enable) begin
            if(reset) q <= 0;
            else    q <= d;
        end
    end
endmodule

//multiplier register
module multreg #(parameter WIDTH=64)
    (input clk,
     input [WIDTH-1:0] a,
     output reg [WIDTH-1:0] b);
    always @(posedge clk) begin
        b <= a;
    end
endmodule

//fetch to decode stage register
module fetchtodec #(parameter WIDTH=32)
    (input clk, reset, enable,
     input [WIDTH-1:0] d0,
     input [WIDTH-1:0] d1,
     output reg [WIDTH-1:0] q0,q1);

```

```
always @(posedge clk) begin
```

```
    if(enable) begin
        q0 <= reset ? 32'b0 : d0;
        q1 <= reset ? 32'b0 : d1;
        /*if(reset) begin q0 <= 0;
            q1 <= 0;
        end
        else begin    q0 <= d0;
            q1 <= d1;
        end*/
    end
end
endmodule
```

```
//decode stage to excute stage register
module dectoexc #(parameter WIDTH=32)
```

```
    (input clk, clear,
     input [WIDTH-1:0] d0, d1,
     input c0,
     input [1:0] c1,
     input c2,
     input [3:0] c3,
     input c4, c5,
     input c6,
     input c7, c8, c9,
     input [4:0] rsd, rtd, rdd,
     input [31:0] signimmd,
     output reg [WIDTH-1:0] q0,q1,
     output reg z0,
     output reg [1:0] z1,
     output reg z2,
     output reg [3:0] z3,
     output reg z4, z5,
     output reg z6,
     output reg z7, z8,z9,
     output reg [4:0] rse, rte,rde,
     output reg [31:0] signimme);
    always @(posedge clk) begin
        if(clear) begin
            {q0, q1, z0, z1, z2, z3, z4, z5, z6, z7, z8, z9,
             rse, rte, signimme} <= 0;
        end
        else begin
            q0 <= d0;
            q1 <= d1;
            z0 <= c0;
            z1 <= c1;
            z2 <= c2;
            z3 <= c3;
            z4 <= c4;
            z5 <= c5;
            z6 <= c6;
            z7 <= c7;
            z8 <= c8;
            z9 <= c9;
            rse <= rsd;
            rte <= rtd;
            rde <= rdd;
            signimme <= signimmd;
        end
    end
endmodule
```

```
// excute to memory register
module exctom #(parameter WIDTH=32)
```

```
    (input clk,
     input [WIDTH-1:0] multih, multlo, aluoutE, writedataE, signimmeE2,
     input [4:0] writeRegE,
     input [1:0] outSelectE,
```

```

        input regWriteE,memtoRegE,memWriteE,
        output reg [WIDTH-1:0] multHiM,multLoM, aluoutM, writedataM, signimmM2,
        output reg [4:0] writeRegM,
        output reg [1:0]outSelectM,
        output reg regWriteM,memtoRegM,memWriteM);
always @(posedge clk) begin
    multHiM <= multHi;
    multLoM <= multLo;
    aluoutM <= aluoutE;
    writedataM <= writedataE;
    signimmM2 <= signimmE2;
    outSelectM <= outSelectE;
    regWriteM <= regWriteE;
    memtoRegM <= memtoRegE;
    memWriteM <= memWriteE;
    writeRegM <= writeRegE;

end

```

endmodule

//mem to write register

```

module mtowrite #(parameter WIDTH=32)
    (input clk,
     input [WIDTH-1:0] readdataM, aluoutM2,
     input [4:0] writeregM,
     input regWriteM,memtoRegM,
     output reg [WIDTH-1:0] readdataW, aluoutW,
     output reg [4:0]writeregW,
     output reg regWriteW,memtoRegW);
always @(posedge clk) begin
    readdataW <= readdataM;
    aluoutW <= aluoutM2;
    writeregW <= writeregM;
    regWriteW <= regWriteM;
    memtoRegW <= memtoRegM;

end

```

endmodule

```

module mux2 #(parameter WIDTH=8)
    (input [WIDTH-1:0] d0, d1,
     input s,
     output [WIDTH-1:0] y);
    assign y = s ? d1 : d0;
endmodule

```

```

module mux3 #(parameter WIDTH=8)
    (input [WIDTH-1:0] d0, d1, d2,
     input [1:0] s,
     output [WIDTH-1:0] y);
    assign y = s[1] ? d2 : (s[0] ? d1 : d0);
endmodule

```

```

module mux4 #(parameter WIDTH=8)
    (input [WIDTH-1:0] d0, d1, d2, d3,
     input [1:0] s,
     output [WIDTH-1:0] y);
    assign y = s[1] ? (s[0] ? d3: d2) : (s[0]? d1 : d0);

```

endmodule

//enable register

```

module enablereg #(parameter WIDTH=8)
    (input clk, enable,

```

```

        input [WIDTH-1:0] d,
        output reg [WIDTH-1:0] q);
    always @(posedge clk) begin
        if(enable) q<=d;
    end
endmodule

//common register
module normalreg #(parameter WIDTH=8)
    (input clk,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk) begin
        q <= d;
    end
endmodule

```

```

module clearreg #(parameter WIDTH = 8)
    (input clk, clear,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);

    always @(posedge clk) begin
        if(clear) q <= 0;
        else q<= d;
    end
endmodule

```

## GeneralMoudleTB.v:

```

module clearreg_tb;

reg clk, clear;
reg [36:0] d;
wire [36:0] q;
clearreg #(37) dut(clk, clear, d, q);

initial begin
    clear <= 0;
    #10;
    d <= 36'd273;
    #10;
    d <= 36'd738;
    #10;
    d <= 36'd15;
    clear <= 1;
    #10;
    d<= 36'd25;
    clear <= 0;
    #10;

end
always begin
    clk <= 1; #5; clk <= 0; #5;
end

endmodule

```

## Hazard\_unit.v:

```

module hazard_unit(input isready, /*input [11:0] opfunc,*/input ismflomfhi,
    input [4:0] RsD, RtD, RsE, RtE,
    input BranchD, input [4:0] WriteRegE, input MemtoRegE, RegWriteE,
    input [4:0] WriteRegM, input MemtoRegM, RegWriteM,
    input [4:0] WriteRegW, input RegWriteW,
    output StallF, StallD, ForwardAD, ForwardBD, FlushE,
    output reg [1:0] ForwardAE, ForwardBE);

```

```

wire lwalld, branchstallD;
// forwarding sources to D stage (branch equality)
assign ForwardAD = (RsD != 0 & RsD == WriteRegM & RegWriteM) ;
assign ForwardBD = (RtD != 0 & RtD == WriteRegM & RegWriteM);
// forwarding sources to E stage (ALU)

//wire ismflomfhi;
//assign ismflomfhi = ((opfunc[11:1] == 11'b00000001001)) /*| (opfunc[11:1] == 11'b00000001100)*;/
always @* begin
    ForwardAE <= 2'b00;
    ForwardBE <= 2'b00;
    if (RsE != 0) begin
        if (RsE == WriteRegM & RegWriteM) begin
            ForwardAE <= 2'b10;
        end
        else if (RsE == WriteRegW & RegWriteW) begin
            ForwardAE <= 2'b01;
        end
    end
    if (RtE != 0) begin
        if (RtE == WriteRegM & RegWriteM) begin
            ForwardBE <= 2'b10;
        end
        else if (RtE == WriteRegW & RegWriteW) begin
            ForwardBE <= 2'b01;
        end
    end
end
end
// stalls
assign lwalld = MemtoRegE & (RtE == RsD | RtE == RtD);

assign branchstallD = BranchD &
    (RegWriteE &
    (WriteRegE == RsD | WriteRegE == RtD) |
    MemtoRegM &
    (WriteRegM == RsD | WriteRegM == RtD));

assign StallD = lwalld | branchstallD | ((~isready) & ismflomfhi);
assign StallF = StallD;
// stalling D stalls all previous stages
assign FlushE = StallD;
// stalling D flushes next stage

endmodule

```

## Data\_path.v:

```

module data_path(input [1:0] pcsrcl, input clk, input rfreset, input se_ze, input eq_ne, input branchd,
    input mul_signd, startmld,
    input [1:0] outseld,
    input regwrited, memtoregd, memwrited,
    input [3:0] alucontrold,
    input alusrcl, regdst,
    output [5:0] opd, output [5:0] functd, output equald);
// fetch
wire [31:0] pcplus4f, pcbranchd, jumpadr, pcnext, pcf, instrf;
//dec
wire [31:0] instrd, pcplus4d, rd1, rd2, immext;
wire [31:0] equaldin1, equaldin2; // for equald input

//exe
wire mul_signe, startmule;
wire [1:0] outsele;
wire regwriree, memtorege, memwritee;
wire [3:0] alucontrole;
wire alusrce, regdste;
wire [31:0] rd1e, rd2e, immexte;
wire [4:0] rse, rte, rde;

```



```

wire [31:0] srcae, srcbe, writedatae;
wire [4:0] writerege;
wire [31:0] immst16;
wire [31:0] aluoute;
wire [63:0] muloute;
wire [63:0] mulregout;

//mem
wire [31:0] aluoutm;
wire [1:0] outselm;
wire regwritem;
wire memtoregm;
wire memwritem;
wire [31:0] writedatam;
wire [4:0] writeregm;
wire [31:0] immextm;
wire [31:0] A;// also called slected aluoutm
wire [31:0] rdm;//readdatam

//wb
wire regwritew;
wire [4:0] writeregw;
wire [31:0] resultw;
wire memtoregw;
wire [31:0] readdataw, aluoutw;
//hazard use
wire stallf, stalld, forwardad,flushe;
wire forwardbd;
wire[1:0] forwardae, forwardbe;
wire isready;
wire ismflomfhi;
assign ismflomfhi = ({instrd[31:26], instrd[5:1]} == 11'b00000001001);
//fetch
mux3 #(32) pcmux(pcpus4f, pcbranchd,jumpadr, pcsrkd, pcnext);

//enablereg #(32) pcreg(clk, ~stallf, pcnext, pcf);
flopr #(32) pcreg(clk, rfreset, ~stallf, pcnext, pcf);
inst_memory i_mem(pcf, instrf); //instruction memory
assign pcpus4f = pcf + 32'b100; // PC+4

fetchtodec f2d(clk, (pcsrkd[0] | pcsrkd[1]), ~stalld,instrf,pcplus4f,instrd,pcplus4d); // fetch to decode stage register
//dec
assign jumpadr = {pcplus4d[31:28],instrd[25:0],2'b00}; // s25I2
assign opd = instrd[31:26]; // op-code
assign functd = instrd[5:0]; //func for control unit
regfile rf(~clk, regwritew, rfreset, instrd[25:21], instrd[20:16], writeregw, resultw, rd1, rd2); //reister file unit
extend ext(instrd[15:0], se_ze, immext); // extent mudoule output as SignImmD labled in the diagram
assign pcbranchd = {immext[29:0], 2'b00} + pcplus4d; // PCBranchD

assign equaldin1 = forwardad ? A : rd1; //2to1 mux for equalD
assign equaldin2 = forwardbd ? A : rd2; //2to1 mux for equalD
assign equald = eq_ne ? (equaldin1 == equaldin2) : (equaldin1 != equaldin2); // the equal compare module
// Decode to excuted stage register
clearreg #(124) d2e(clk, flushe, {mul_signd,startmuld,outsele,regwrited, memtoregd,
memwrited,alucontrold,alusrkd,regdstd,rd1,rd2,instrd[25:21],instrd[20:16],instrd[15:11],immext},
{mul_signe,startmule,outsele,regwritew, memtorege,
memwritew,alucontrole,alusrce,regdste,rd1e,rd2e,rse,rte,rde,immexte});
assign writerege = regdste ? rde : rte;// 2to1 mux for writeRegE
assign srcae = forwardae[1] ? A : (forwardae[0] ? resultw : rd1e);// 3to1 mux for srcAE
assign writedatae = forwardbe[1] ? A : (forwardbe[0] ? resultw : rd2e);// 3to1 mux for WriteDataE
assign srcbe = alusrce ? immexte : writedatae;// 2to1 mux for SrcBE
ALU aluodule(srcae, srcbe,alucontrole,aluoute);// ALU moudle
//multiplier multmodule(srcae, srcbe, clk, startmule,mul_signe,muloute);// Multiplier module
laji_mult multmodule(srcae, srcbe, clk, rfreset, startmule, mul_signe, muloute, isready);
assign mulregout = muloute; // Multiplier register
//multreg multregmodule(clk, muloute, mulregout);
// excution to memory stage register
normalreg #(106) e2m(clk, {outsele, regwritew,memtorege,memwritew,aluoute,writedatae,writerege,immexte[15:0],16'b0},
{outselm, regwritem,memtoregm,memwritem,aluoutm,writedatam,writeregm,immextm});
//4-1 Mux for Data Memory input A

```

```

mux4 #(32) aluoutmmux(mulregout[63:32],mulregout[31:0],aluoutm,immextm,outselm,A);
data_memory dmem(clk, memwritem, A, writedatam, rdm);// Data Memory module
//Memory to WriteBack stage register
normalreg #(71) m2w(clk,{regwritem,memtoregm,rdm,A,writeregm},{regwritew,memtoregw,readdataw,aluoutw,writeregw});
assign resultw = memtoregw ? readdataw : aluoutw;
// Hazard Unit
hazard_unit hazardmodule((isready & ~startmule), ismflomfhi,
instrd[25:21],instrd[20:16],rse,rte,branchd,writerege,memtorege,regwritew,writeregw,regwritew,stallf,stall
d,forwardad,forwardbd,flushd,forwardae,forwardbe);

```

```
endmodule
```

## datapath\_tb.v:

```

module datapath_tb;
    reg clk;
    reg reset;

    top dut(clk, reset);

    initial begin
        reset <= 1; #22; reset <= 0;
        #5000;
        $stop;
    end

    always begin
        clk <= 1; #5; clk <= 0; #5;
    end

endmodule

```

## Mips.v:

```

module tb;
    reg clk;
    reg reset;

    top dut(clk, reset);

    initial begin
        reset <= 1; #22; reset <= 0;
        #5000;
        $stop;
    end

    always begin
        clk <= 1; #5; clk <= 0; #5;
    end

endmodule

```

## multiplier.v:

```

module laji_mult(input [31:0] a, input [31:0] b, input clk, input reset, input start, input is_signed, output [63:0] s, output reg isready);

    reg [63:0] Asign;
    reg [31:0] Bsign;

```

```

reg [63:0] outsigned;

reg [31:0] laji_counter;
assign s = outsigned;
always @(posedge clk) begin
    if(reset) begin
        laji_counter <= 0;
        isready <= 1;
        outsigned <= 0;
    end
    if(start) begin
        laji_counter <= 32;
        Asign <= is_signed ? {{32{a[31]}}}, a} : {32'b0,a};
        Bsign <= b;
        outsigned <= 0;
        isready <= 0;
    end
    else if(laji_counter > 1) begin
        if(Bsign[32-laji_counter]) outsigned <= outsigned + Asign;
        else outsigned <= outsigned;
        Asign <= {Asign[62:0],1'b0};
        laji_counter <= laji_counter - 1;
        if(laji_counter == 3) isready <= 1;
    end
    else if(laji_counter == 1) begin
        if(Bsign[32-laji_counter]) outsigned <= outsigned - Asign;
        else outsigned <= outsigned;
        Asign <= {Asign[62:0],1'b0};
        laji_counter <= laji_counter - 1;
        //isready <= 1;
    end
end
end
endmodule

```

## mult\_tb.v:

```

module mult_tb();
    reg clk;
    reg start;
    reg is_signed;
    reg reset;
    wire [63:0] s;
    wire isready;
    reg [31:0] a,b;

    always begin
        clk <= 1;#5;clk<=0;#5;
    end
    laji_mult dut (a,b, clk,reset, start, is_signed,s, isready);
    initial begin
        start <= 0;
        reset <= 1;
        #10;
        reset <= 0;
        #20;
        a <= 20;
        b <= 30;
        is_signed <= 0;
        start <= 1;
        #10
        start<=0;
        #320;
        start <= 1;
        a <= 24;
        b <= 311;
        is_signed <= 0;
        #10;
        start <= 0;
    end
endmodule

```

```

#320;
start <= 1;
a <= -24;
b <= 311;
is_signed <= 0;
#10;
start <= 0;
#320;
start <= 1;
a <= -24;
b <= 311;
is_signed <= 1;
#10;
start <= 0;
#320;
start <= 1;
a <= 311;
b <= -24;
is_signed <= 1;
#10;
start <= 0;
#320;

```

```

$stop;

```

```

end

```

```

//always begin
//    clk <= 1;#5;clk<=0;#5;
//end

```

```

endmodule

```

## reg\_file.v:

```

module regfile(input clk,
    input Write,
    input Reset,
    input [4:0] PR1, PR2, WR,
    input [31:0] WD,
    output [31:0] RD1, RD2);

    reg [31:0] rf[31:0];

    always @(posedge clk) begin

        if ( Write && ~Reset) rf[WR] <= WD;

        if(Reset) begin

            rf[0] = 32'b0;
            rf[1] = 32'b0;
            rf[2] = 32'b0;
            rf[3] = 32'b0;
            rf[4] = 32'b0;
            rf[5] = 32'b0;
            rf[6] = 32'b0;
            rf[7] = 32'b0;
            rf[8] = 32'b0;
            rf[9] = 32'b0;
            rf[10] = 32'b0;
            rf[11] = 32'b0;
            rf[12] = 32'b0;
            rf[13] = 32'b0;
            rf[14] = 32'b0;
            rf[15] = 32'b0;

```

```

rf[16] = 32'b0;
rf[17] = 32'b0;
rf[18] = 32'b0;
rf[19] = 32'b0;
rf[20] = 32'b0;
rf[21] = 32'b0;
rf[22] = 32'b0;
rf[23] = 32'b0;
rf[24] = 32'b0;
rf[25] = 32'b0;
rf[26] = 32'b0;
rf[27] = 32'b0;
rf[28] = 32'b0;
rf[29] = 32'b11111100;
rf[30] = 32'b0;
rf[31] = 32'b0;

```

```

end
end

```

```

assign RD1 = (PR1 != 0) ? rf[PR1] : 0;
assign RD2 = (PR2 != 0) ? rf[PR2] : 0;
endmodule

```

## reg\_file\_tb.v:

```

module reg_file_tb();
    reg clk;
    reg Write;
    reg Reset;
    reg [4:0] PR1, PR2, WR;
    reg [31:0] WD;
    wire [31:0] RD1, RD2;
    always begin
        clk <= 1;#5;clk<=0;#5;
    end
    regfile dut(clk, Write, Reset, PR1, PR2, WR, WD, RD1, RD2);
    initial begin
        Write <= 0;
        Reset <= 1;
        WR <= 5'b01011;
        WD <= 32'b 0010101;
        PR1 <= 5'b01000;
        PR2 <= 5'b01010;
        #10
        Write <= 1;
        Reset <= 0;
        WR <= 5'b01111;
        WD <= 32'b 0010101;
        PR1 <= 5'b01000;
        PR2 <= 5'b01011;
        #10
        Write <= 1;
        Reset <= 0;
        WR <= 5'b01000;
        WD <= 32'b 0010101;
        PR1 <= 5'b01000;
        PR2 <= 5'b01011;
        #10
        Write <= 1;
        Reset <= 1;
        WR <= 5'b01000;
        WD <= 32'b 0010101;
        PR1 <= 5'b01000;
        PR2 <= 5'b01011;
        #10
        $stop;
    end
endmodule

```

```
end  
endmodule
```

## Top.v:

```
module top(input clk, reset);  
    wire [31:0] pc, instr, readdata;  
    wire [31:0] aluout, writedata;  
    wire      memWrite;  
  
    // processor and memories are instantiated here  
    mips mip(clk, reset, pc,/*instr,*/memWrite,  
            aluout, writedata, readdata);  
endmodule
```